



Notes:

- \* Max 12v for the IRF540. If you want to increase the input voltage, use a better MOSFET such as IRFP250 or IRFP450.
- \* The Failsafe Resistor is optional, however it will save your MOSFET from frying if your 555 timer should fail.
- \*The resonance capacitor is experimental, use different values to achieve the results. I found 680nF works the best for me.

By Plasmana